

Linearized 5-GHz Power Amplifier for 11ac 160-MHz Non-Continuous Channel




Date: 2012-01-17

Authors:


Name	Affiliations	Address	Phone	email
Tian-Wei Huang	National Taiwan University	No. 1, Sec. 4, Roosevelt Road, Taipei, 10617 Taiwan(R.O.C.)	+886-2-33665084	twhuang@cc.ee.ntu.edu.tw
Hong-Yuan Yang,	National Taiwan University	No. 1, Sec. 4, Roosevelt Road, Taipei, 10617 Taiwan(R.O.C.)	+886-2-33665084	bays1977@gmail.com
Vish Ponnampalam	Media Tek	No.1, Dusing Rd. 1, Hsinchu Science Park, Hsin-Chu, Taiwan 30078, R.O.C.	+886-3-567-0766	vish.ponnampalam@mediatek.com

160 MHz Non-Adjacent Channel Possible Interference

doc.: IEEE 802.11-11/0325r0

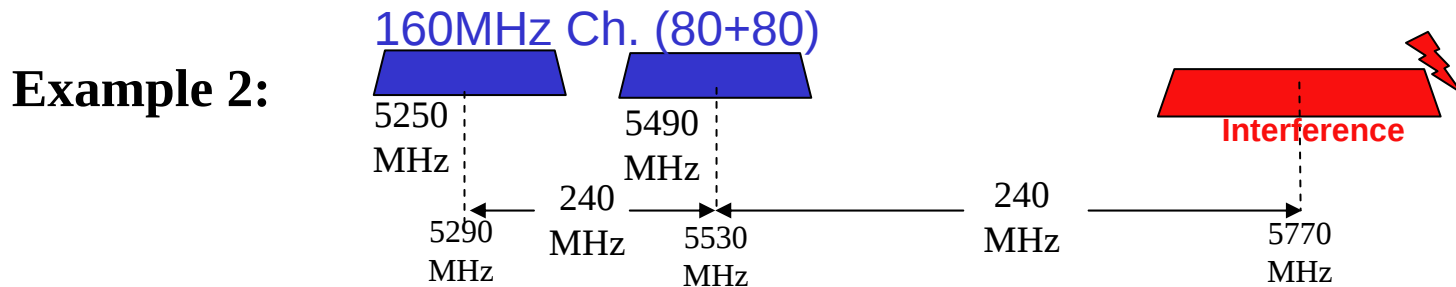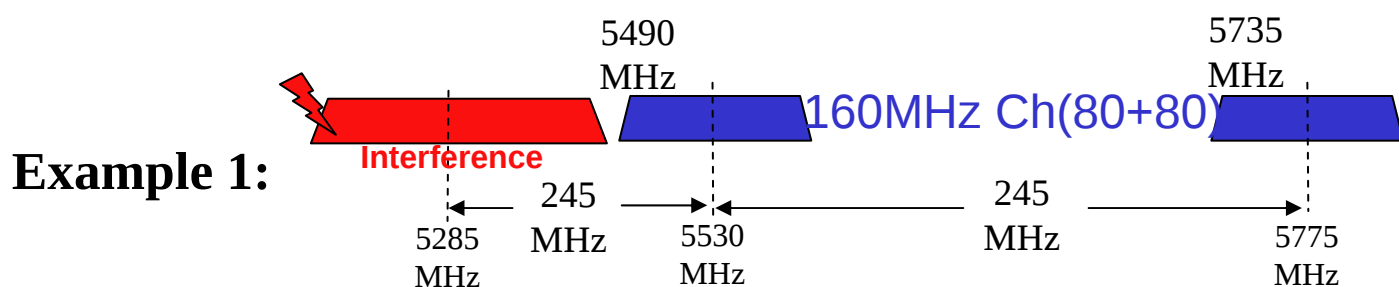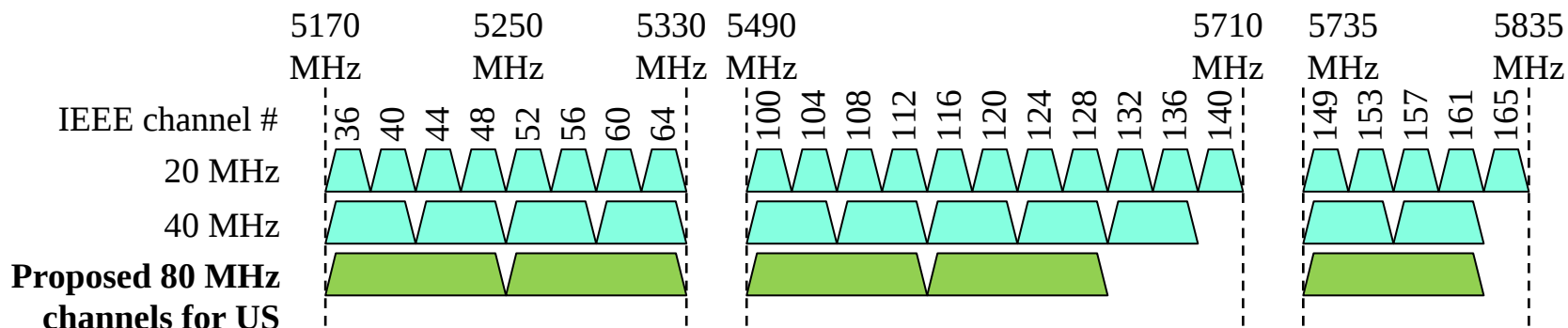

Example 2

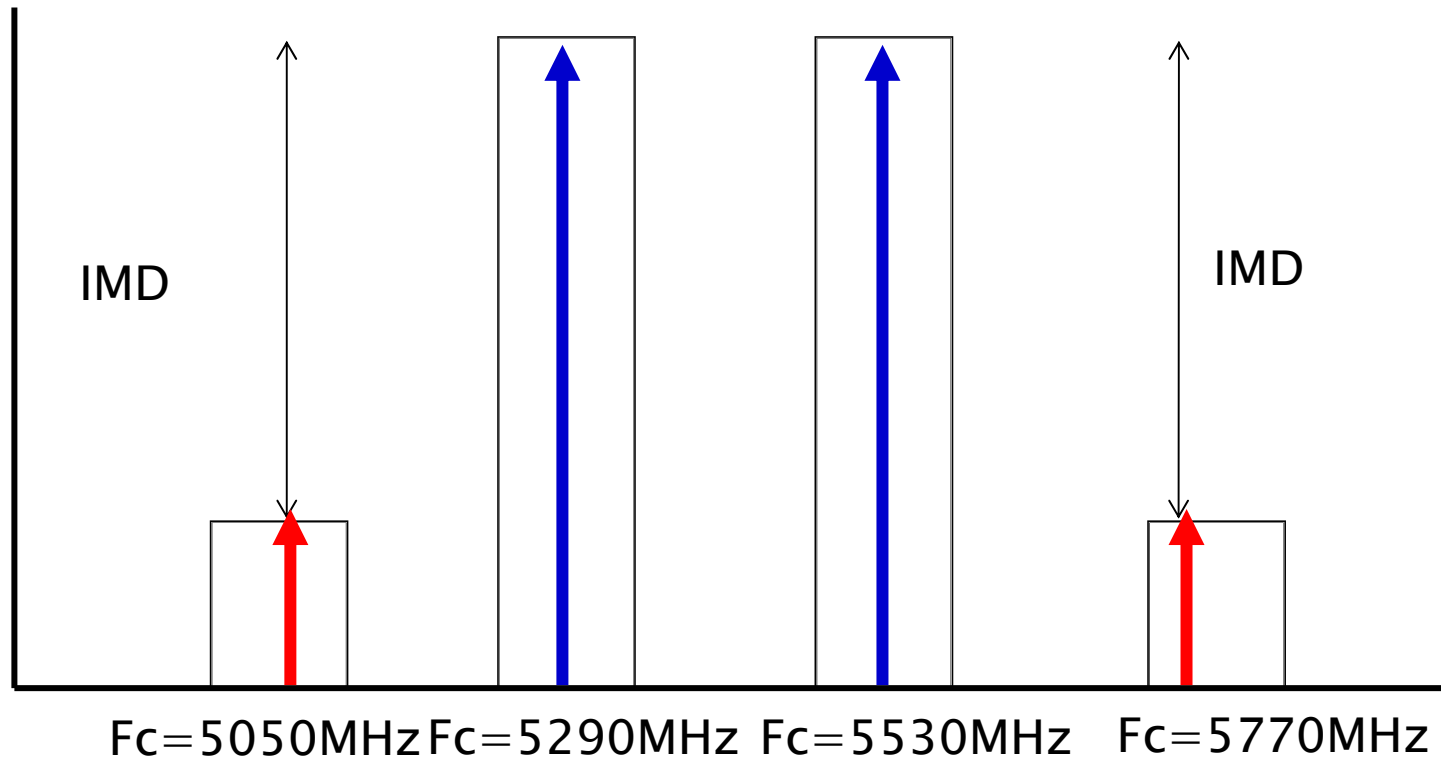


Transistors Characteristics

ATF-33143

Low Noise Pseudomorphic HEMT in a Surface Mount Plastic Package


ATF-33143 Model

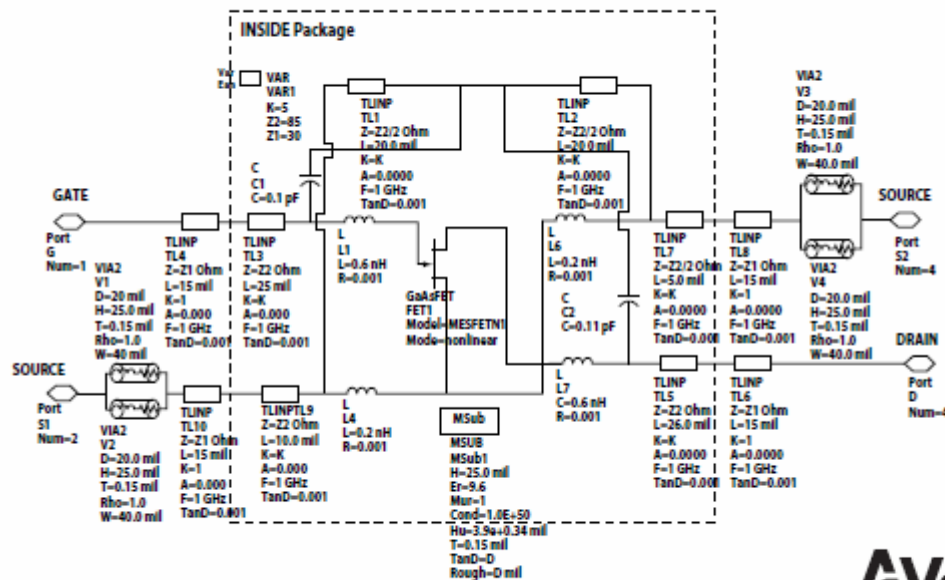

AVAGO
TECHNOLOGIES

<http://www.avagotech.com>

Surface Mount Package SOT-343

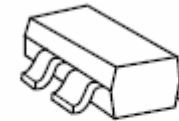

Pin Connections and Package Marking



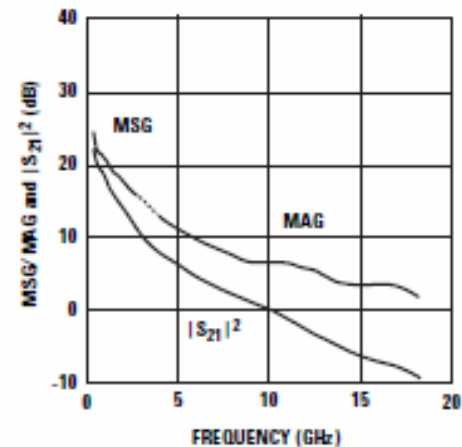
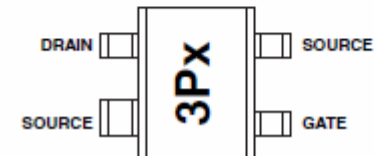


Figure 26. MSG/MAG and $|S_{21}|^2$ vs. Frequency at 4V, 80 mA.

Main Amplifier S-parameters

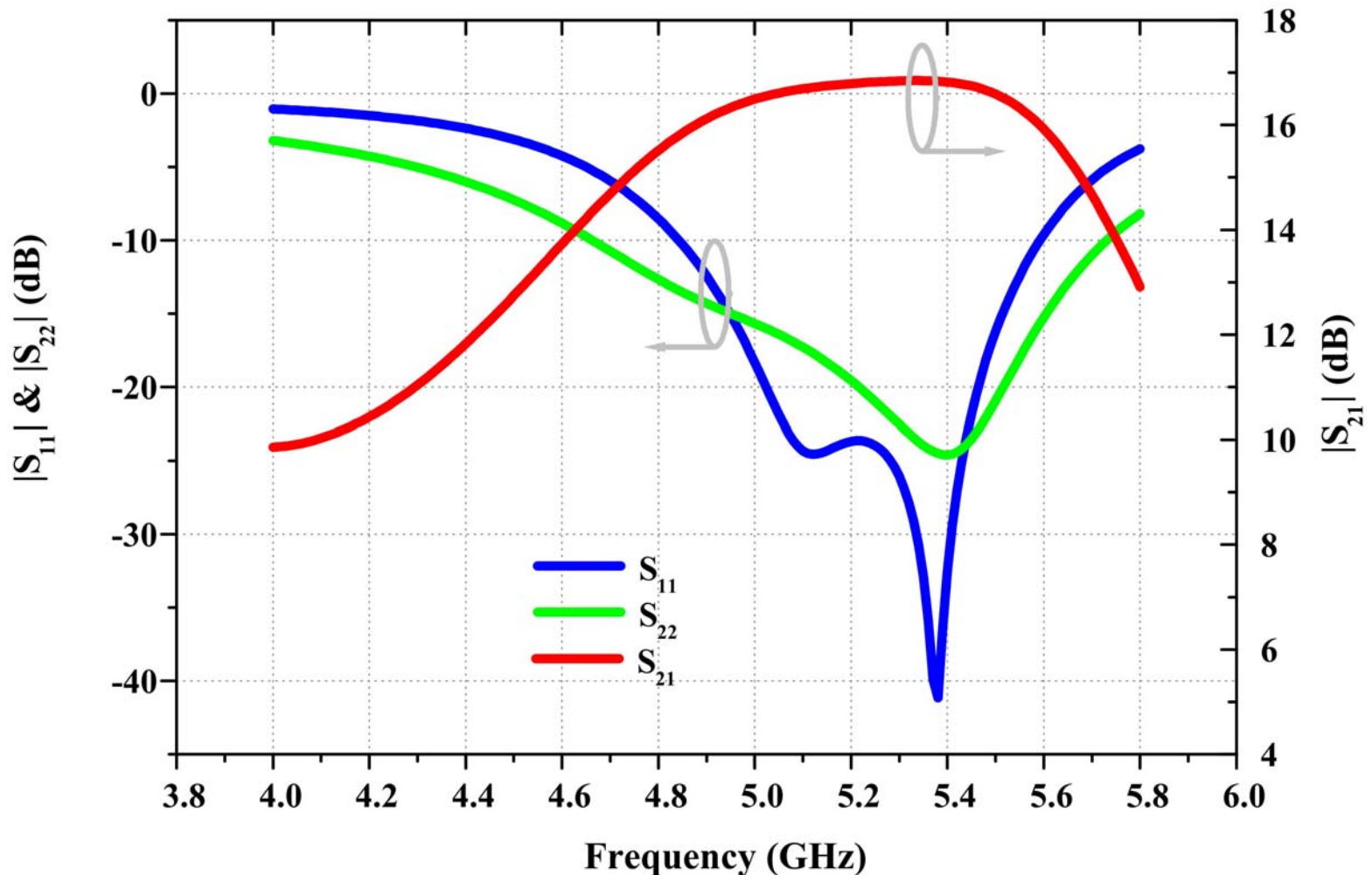


Two-tone Simulation (Example 2)

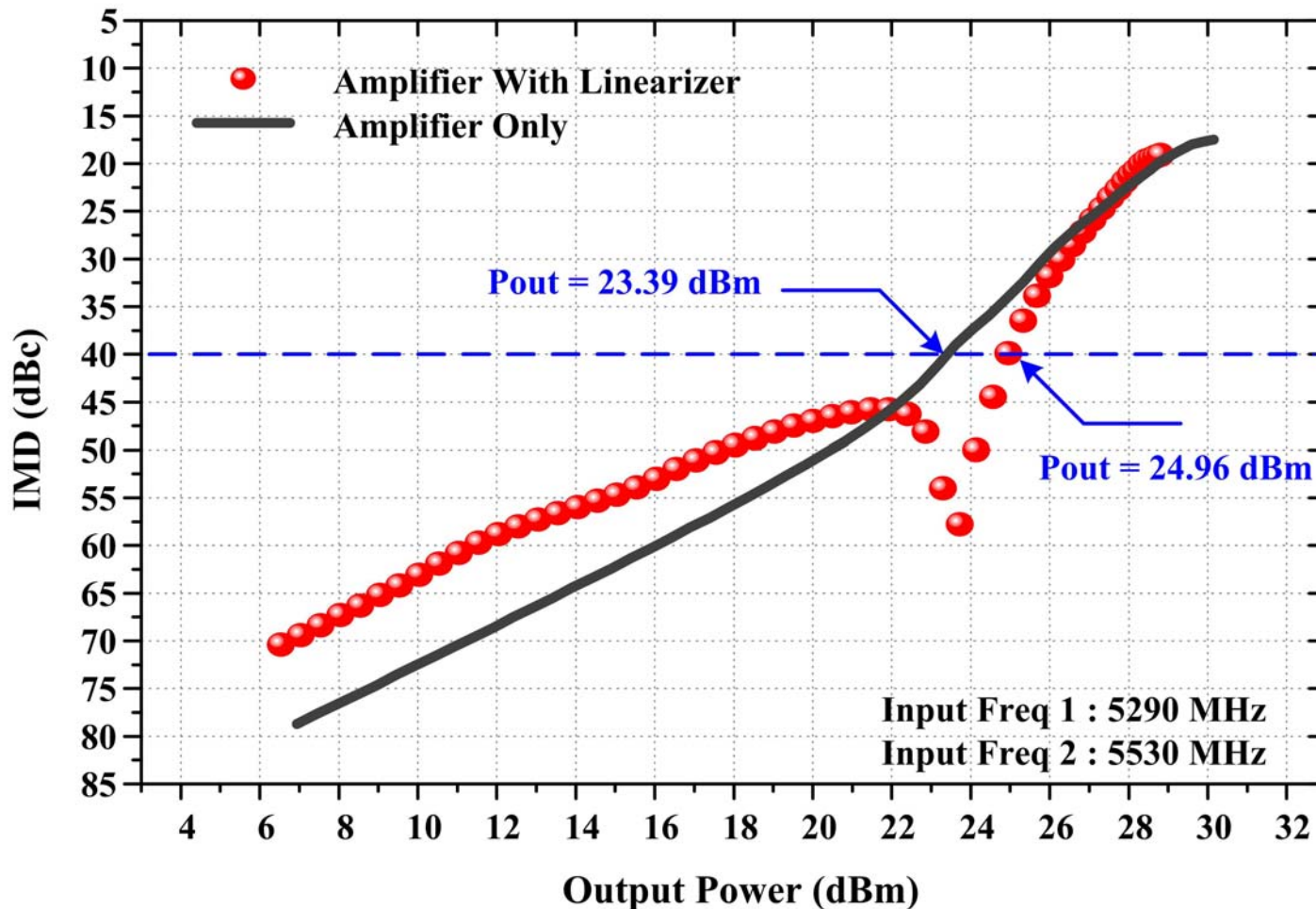

IMD : Intermodulation Distortion Ratio

Large Signal Simulation

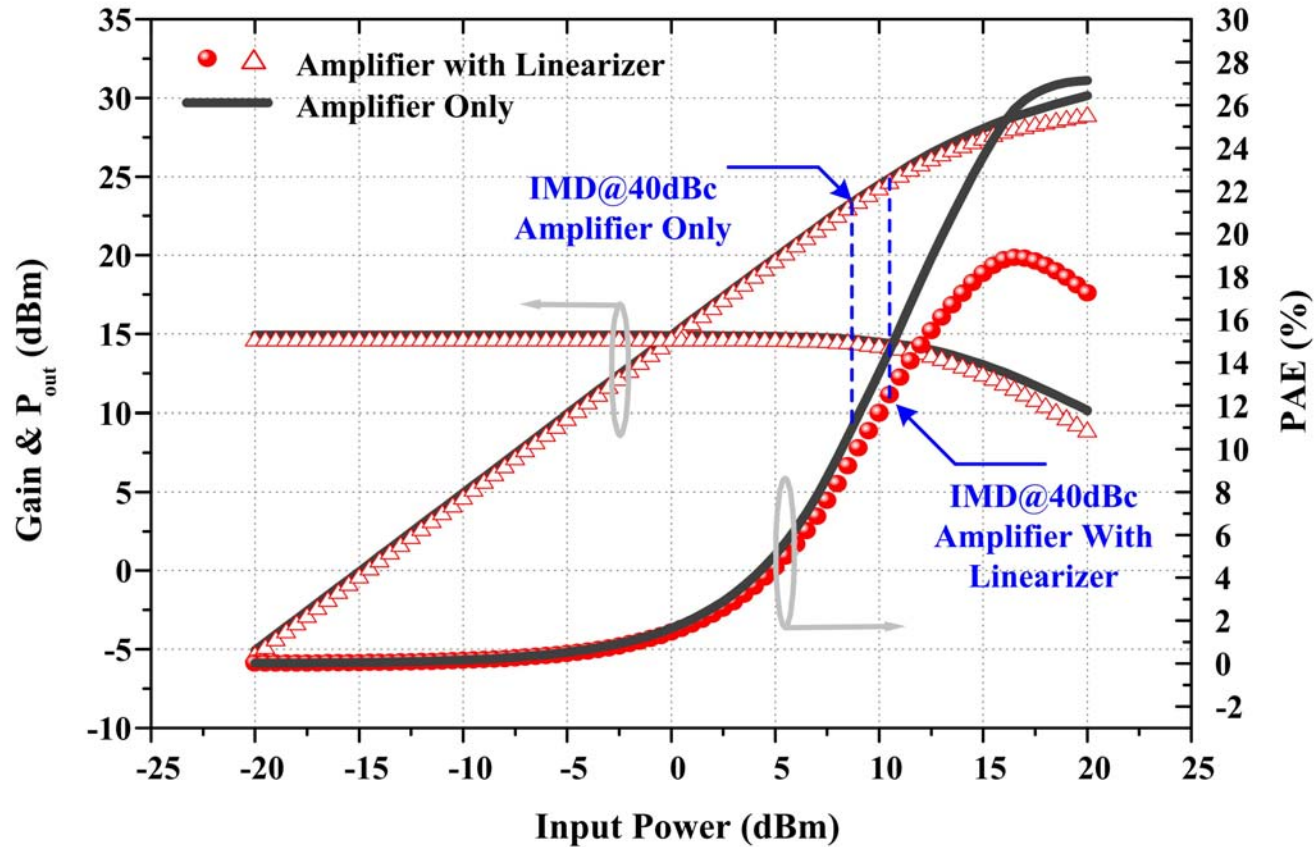

IMD@40 dBc	Pin (dBm)	Pout (dBm)	Gain (dB)	PAE (%)
Amplifier Only	8.75	23.39	14.64	11.08
Amplifier With Linearizer	11	24.96	13.96	13.30

Conclusion

- **For IMD@-40dBc spec.**
 - Pout: OP1dB-4dBm (Amplifier only)
 - Pout: OP1dB-2dBm (Amplifier with Linearizer)

- **5-GHz Linearizer creates ‘Sweet Spot’ to increase linear power more close to saturation with higher efficiency.**